

# Trabalho Final

raiz quadrada por busca binária

# Algoritmo

```
def sqrt_binary_search(x):  
  
    start = 0  
    end = x  
    cont = 0  
  
    while start <= end:  
  
        mid = (start+end)//2  
        cont = cont + 1  
  
        if x == mid * mid:  
            break  
        elif x < mid * mid:  
            end = mid - 1  
        elif x > mid * mid:  
            start = mid + 1  
  
    print("cont: " + str(cont))  
    return end  
  
while 1:  
    print("resultado: " + str(sqrt_binary_search(int(input()))))
```

Num = 64, start = 0, end = 64

Mid = 32, como  $32 * 32 > 64$  end = 31

Mid = 15,  $15 * 15 > 64$  end = 14

Mid = 7,  $7 * 7 < 64$  start = 8 end = 14

Mid =  $(8+14)//2 = 11$ ,  $11 * 11 > 64$  end = 10

Mid = 9,  $9 * 9 > 64$ , end = 8

Como  $8*8 == 64$ , saímos do while retornando o valor de end, que no momento está em 8, finalizando assim a operação.

# Algoritmo

Num = 10, start = 0, end = 10

Mid = 5, como  $5 * 5 > 10$  end = 4

Mid = 2,  $2 * 2 < 10$  start = 3

Mid = 3,  $3 * 3 < 10$  start = 4 end = 3

Como start > end, devemos sair do programa e retornar end que é 3 e seria o valor aproximado para raiz de 10.

Mostrando desempenho do algoritmo em casos que possuem raízes não exatas.

```
def sqrt_binary_search(x):
```

```
    start = 0
    end = x
    cont = 0
```

```
    while start <= end:
```

```
        mid = (start+end)//2
        cont = cont + 1
```


```
        if x == mid * mid:
            break
        elif x < mid * mid:
            end = mid - 1
        elif x > mid * mid:
            start = mid + 1
```

```
    print("cont: " + str(cont))
    return end
```


```
while 1:
    print("resultado: " + str(sqrt_binary_search(int(input()))))
```
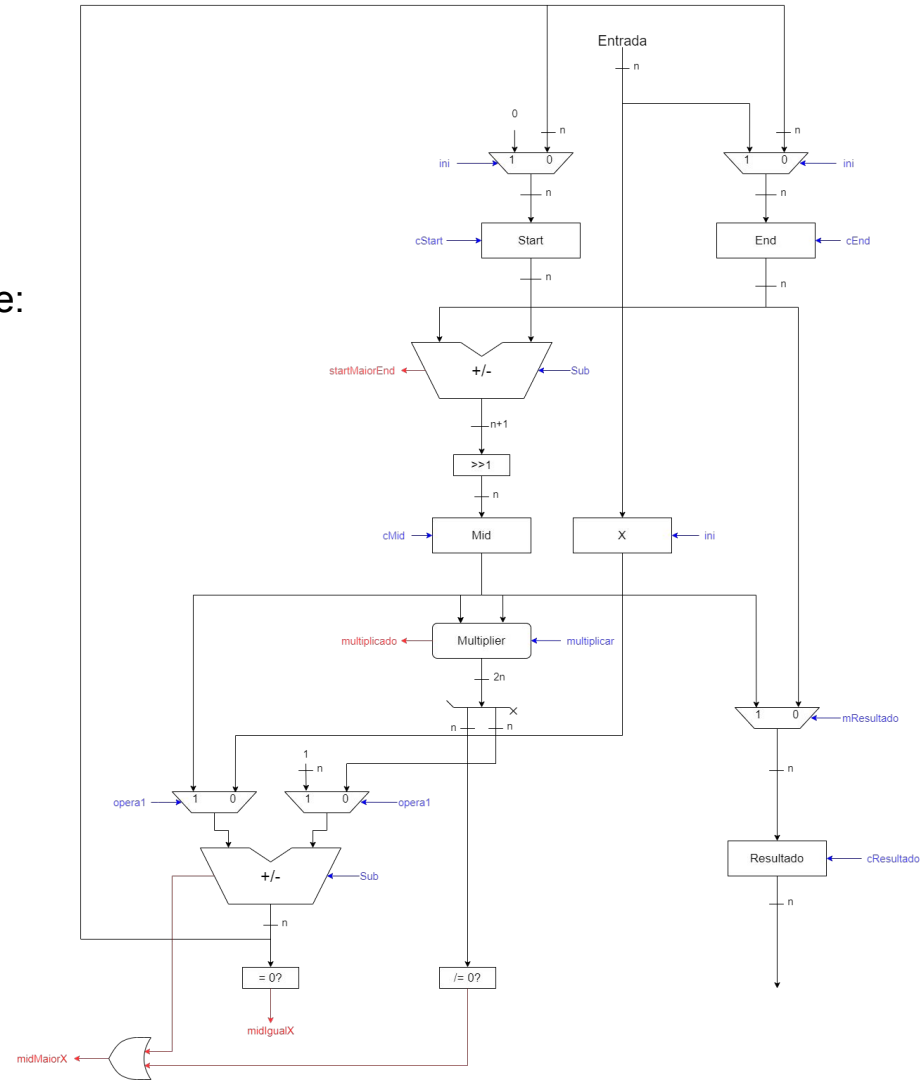
## Arquiteturas (diagramas de blocos do B0)

Transformando o algoritmo em arquitetura chegamos ao seguinte:



# Máquina de Estados

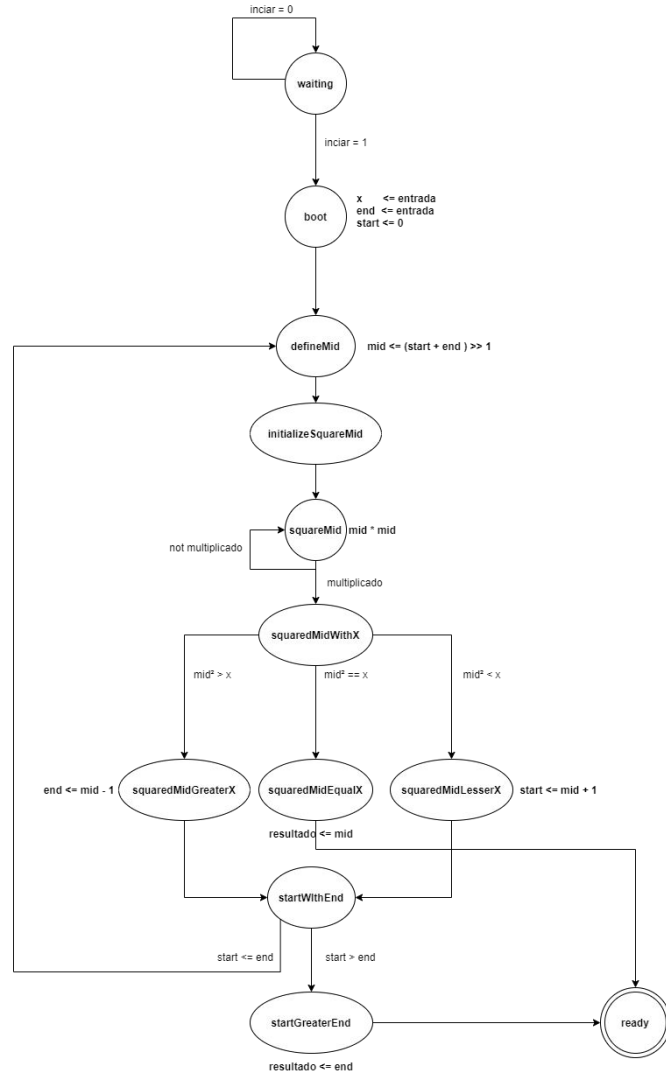

# Máquina de Estados

	ini	cStart	cEnd	cMid	cResultado	sub	multiplicar	mResultado	opera1	pronto
waiting	0	-	-	-	-	-	0	-	-	0
boot	1	1	1	-	-	-	0	-	-	0
defineMid	0	0	0	1	-	0	0	-	-	0
initializeSquareMid	0	0	0	0	-	-	1	-	-	0
squareMid	0	0	0	0	-	-	0	-	-	0
squaredMidWithX	0	0	0	0	-	1	0	-	0	0
squaredMidGreaterX	0	0	1	0	-	1	0	-	1	0
squaredMidEqualX	-	-	-	-	1	-	-	1	-	0
squaredMidLesserX	0	1	0	0	-	0	0	-	1	0
startWithEnd	0	0	0	0	-	1	0	-	-	0
startGreaterEnd	-	-	-	-	1	-	-	0	-	0
ready	-	-	-	-	0	-	-	-	-	1

# VHDS - BC

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity sqrt_bc is
    port(clk, reset, iniciar,
          multiplicado, startMaiorEnd, midMaiorX, midIguarX : in std_logic;
          ini, cStart, cEnd, cMid, cResultado, sub, multiplicar, mResultado, opera1, pronto : out std_logic);
end sqrt_bc;
```

architecture arch of sqrt\_bc is

```
    type states is (waiting, boot, defineMid, initializeSquareMid, squareMid, squaredMidWithX, squaredMidGreaterX, squaredMidEqualX,
                    squaredMidLesserX, startWithEnd, startGreaterEnd, ready);
    signal state, nextState : states;
```

```
begin
    ChangeOfState : process (clk, reset)
    begin
        if reset = '1' then
            state <= waiting;
        elsif rising_edge(clk) then
            state <= nextState;
```

```
        end if;
    end process;
```

```
    LogicalOfStates : process (state, iniciar, multiplicado, midMaiorX, midIguarX, startMaiorEnd)
    begin
        case state is
            when waiting =>
                if iniciar = '0' then
                    nextState <= waiting;
                else
                    nextState <= boot;
                end if;
            when boot =>
                nextState <= defineMid;
            when defineMid =>
                nextState <= initializeSquareMid;
            when initializeSquareMid =>
                nextState <= squareMid;
            when squareMid =>
                if multiplicado = '0' then
                    nextState <= squareMid;
                else
                    nextState <= squaredMidWithX;
                end if;
```

```
            when squaredMidWithX =>
                if midMaiorX = '1' then
                    nextState <= squaredMidGreaterX;
                elsif midIguarX = '1' then
                    nextState <= squaredMidEqualX;
                else
                    nextState <= squaredMidLesserX;
                end if;
            when squaredMidGreaterX =>
                nextState <= startWithEnd;
            when squaredMidEqualX =>
                nextState <= ready;
            when squaredMidLesserX =>
                nextState <= startWithEnd;
            when startWithEnd =>
                if startMaiorEnd = '1' then
                    nextState <= startGreaterEnd;
                else
                    nextState <= defineMid;
                end if;
            when startGreaterEnd =>
                nextState <= ready;
            when others =>
                nextState <= ready;
        end case;
    end process;
end process;
OutputSignals : process (state)
begin
    case state is
        when waiting =>
            ini <= '0';
            cStart <= '1';
            cEnd <= '1';
            cMid <= '1';
            cResultado <= '1';
            sub <= '1';
            multiplicar <= '0';
            mResultado <= '1';
            opera1 <= '1';
            pronto <= '0';
        when boot =>
            ini <= '1';
            cStart <= '1';
            cEnd <= '1';
            cMid <= '1';
            cResultado <= '1';
            sub <= '1';
            multiplicar <= '0';
            mResultado <= '1';
            opera1 <= '1';
            pronto <= '0';
        when defineMid =>
            ini <= '0';
            cStart <= '0';
            cEnd <= '0';
            cMid <= '1';
            cResultado <= '1';
            sub <= '0';
            multiplicar <= '0';
            mResultado <= '1';
            opera1 <= '1';
            pronto <= '0';
```

when initializeSquareMid =>

```
ini      <= '0';
cStart   <= '0';
cEnd     <= '0';
cMid     <= '0';
cResultado <= '1';
sub      <= '1';
multiplicar <= '1';
mResultado <= '1';
opera1   <= '1';
pronto   <= '0';
```

when squareMid =>

```
ini      <= '0';
cStart   <= '0';
cEnd     <= '0';
cMid     <= '0';
cResultado <= '1';
sub      <= '1';
multiplicar <= '0';
mResultado <= '1';
opera1   <= '1';
pronto   <= '0';
```

when squaredMidWithX =>

```
ini      <= '0';
cStart   <= '0';
cEnd     <= '0';
cMid     <= '0';
cResultado <= '1';
sub      <= '1';
multiplicar <= '0';
mResultado <= '1';
opera1   <= '0';
pronto   <= '0';
```

when squaredMidGreaterX =>

```
ini      <= '0';
cStart   <= '0';
cEnd     <= '1';
cMid     <= '0';
cResultado <= '1';
sub      <= '1';
multiplicar <= '0';
mResultado <= '1';
opera1   <= '1';
pronto   <= '0';
```

when squaredMidEqualX =>

```
ini      <= '1';
cStart   <= '1';
cEnd     <= '1';
cMid     <= '1';
cResultado <= '1';
sub      <= '1';
multiplicar <= '1';
mResultado <= '1';
opera1   <= '1';
pronto   <= '0';
```

when squaredMidLesserX =>

```
ini      <= '0';
cStart   <= '1';
cEnd     <= '0';
cMid     <= '0';
cResultado <= '1';
sub      <= '0';
multiplicar <= '0';
mResultado <= '1';
opera1   <= '1';
pronto   <= '0';
```

when startWithEnd =>

```
ini      <= '0';
cStart   <= '0';
cEnd     <= '0';
cMid     <= '0';
cResultado <= '1';
sub      <= '1';
multiplicar <= '0';
mResultado <= '1';
opera1   <= '1';
pronto   <= '0';
```

when startGreaterEnd =>

```
ini      <= '1';
cStart   <= '1';
cEnd     <= '1';
cMid     <= '1';
cResultado <= '1';
sub      <= '1';
multiplicar <= '1';
mResultado <= '0';
opera1   <= '1';
pronto   <= '0';
```

when others =>

```
ini      <= '1';
cStart   <= '1';
cEnd     <= '1';
cMid     <= '1';
cResultado <= '0';
sub      <= '1';
multiplicar <= '1';
mResultado <= '1';
opera1   <= '1';
pronto   <= '1';
```

end case;

end process;

end arch;



# BO

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
```

```
entity sqrt_bo is
generic(n : natural);
port(clk, reset,
      ini, cStart, cEnd, cMid, cResultado, sub, multiplicar, mResultado, opera1 : in std_logic;
      entrada : in std_logic_vector(n-1 downto 0);
      multiplicado, startMaiorEnd, midMaiorX, midIgualX : out std_logic;
      saida : out std_logic_vector(n-1 downto 0));
end sqrt_bo;
```

architecture estrutura of sqrt\_bo is

```
COMPONENT registrador IS
generic (n : natural);
PORT (clk, carga : IN STD_LOGIC;
      d : IN STD_LOGIC_VECTOR(n-1 DOWNT0 0);
      q : OUT STD_LOGIC_VECTOR(n-1 DOWNT0 0));
```

END COMPONENT;

```
COMPONENT mux2para1 IS
generic (n : natural);
PORT (a, b : IN STD_LOGIC_VECTOR(n-1 DOWNT0 0);
      sel : IN STD_LOGIC;
      y : OUT STD_LOGIC_VECTOR(n-1 DOWNT0 0));
```

END COMPONENT;

```
COMPONENT somadorsubtrator IS
generic (n : natural);
PORT (a, b : IN STD_LOGIC_VECTOR(n-1 DOWNT0 0);
      op : IN STD_LOGIC;
      Cout : OUT STD_LOGIC;
      s : OUT STD_LOGIC_VECTOR(n-1 DOWNT0 0));
```

END COMPONENT;

```
COMPONENT igualazero IS
generic (n : natural);
PORT ( a : IN STD_LOGIC_VECTOR(n-1 DOWNT0 0);
      igual : OUT STD_LOGIC);
```

END COMPONENT;

```
COMPONENT diferentezero IS
generic (n:natural);
PORT ( a : IN STD_LOGIC_VECTOR(n-1 DOWNT0 0);
      diferente : OUT STD_LOGIC);
END COMPONENT;
```

```
COMPONENT multiplier2 is
generic (n:natural);
port(entA, entB : in std_logic_vector(n-1 downto 0);
      iniciar, Reset, ck :in std_logic;
      pronto : out std_logic;
      mult : out std_logic_vector((2*n)-1 downto 0)
);
```

END COMPONENT;

```
signal saidaSTART, saidaMID, saidaEND, saidaX, saidaSOMASUB_StartEnd, saidaSOMASUB_MidX, saidaSOMASUB_StartEndShifted,
saidaMuxSTART, saidaMuxEND, saidaMuxRESULTADO, saidaMuxMidX, saidaMuxMidOne,
zero : std_logic_vector(n-1 downto 0);
signal saidaMULT : std_logic_vector(2*n-1 downto 0);
signal coutStartEnd, coutMidX, midMaiorXPorBits : std_logic;
```

```
begin
X : registrador
generic map (n => n)
port map(clk, ini, entrada, saidaX);

Start : registrador
generic map (n => n)
port map(clk, cStart, saidaMuxSTART, saidaSTART);
```

```
Mid : registrador
generic map (n => n)
port map(clk, cMid, saidaSOMASUB_StartEndShifted, saidaMID);
```

```
End_r : registrador
generic map (n => n)
port map(clk, cEND, saidaMuxEND, saidaEND);
```

```
Resultado : registrador
generic map (n => n)
port map(clk, cResultado, saidaMuxRESULTADO, saida);
```

```
muxStart : mux2para1
generic map (n => n)
port map(saidaSOMASUB_MidX, (others => '0'), ini, saidaMuxSTART);
```

```
muxEnd : mux2para1
generic map (n => n)
port map(saidaSOMASUB_MidX, entrada, ini, saidaMuxEND);
```

```
muxMidX : mux2para1
generic map (n => n)
port map(saidaX, saidaMID, opera1, saidaMuxMidX);
```

```
muxMidOne : mux2para1
generic map (n => n)
port map(saidaMULT(n-1 downto 0), ((0) => '1', others => '0'), opera1, saidaMuxMidOne);
```

```
muxResultado : mux2para1
  generic map (n => n)
  port map(saidaEND, saidaMID, mResultado, saidaMuxRESULTADO);

SomaSub_StartEnd : somadorsubtrator
  generic map (n => n)
  port map(saidaEND, saidaSTART, sub, coutStartEnd, saidaSOMASUB_StartEnd);
saidaSOMASUB_StartEndShifted <= coutStartEnd & saidaSOMASUB_StartEnd(n-1 downto 1);
startMaiorEnd <= coutStartEnd;

SomaSub_MidX : somadorsubtrator
  generic map (n => n)
  port map(saidaMuxMidX, saidaMuxMidOne, sub, coutMidX, saidaSOMASUB_MidX);

StartIguarX : igualazero
  generic map (n => n)
  port map(saidaSOMASUB_MidX, midIguarX);

Multiplier : multiplier2
  generic map (n => n)
  port map(saidaMID, saidaMID, multiplicar, reset, clk, multiplicado, saidaMULT);


MidGreaterThanNBits : diferentezero
  generic map (n => n)
  port map(saidaMULT(2*n-1 downto n), midMaiorXPorBits);

midMaiorX <= coutMidX or midMaiorXPorBits;

end estrutura;
```


# Netlists

## Bloco operativo 8 bits

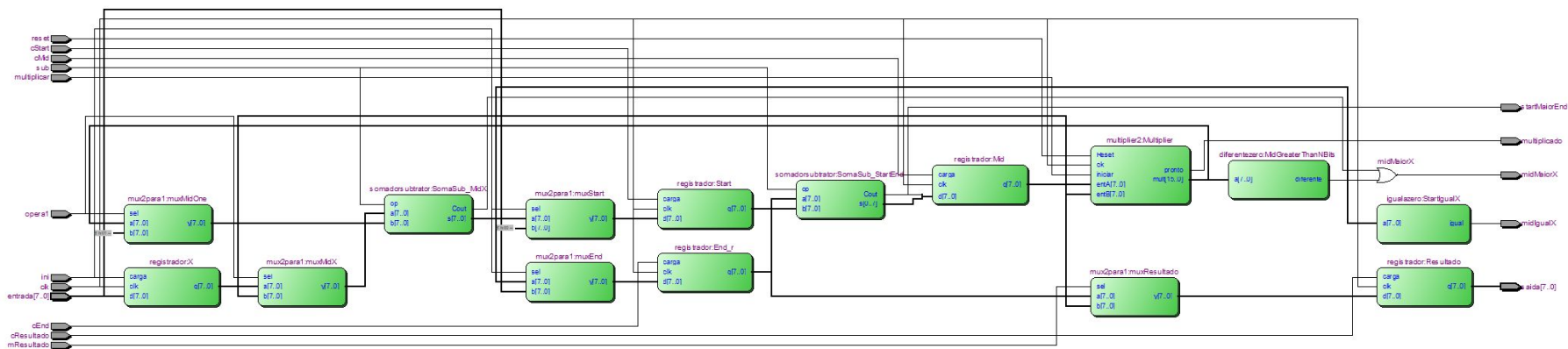


# Netlists

## Bloco operativo 4 bits

 

# Netlists

## Bloco de Controle

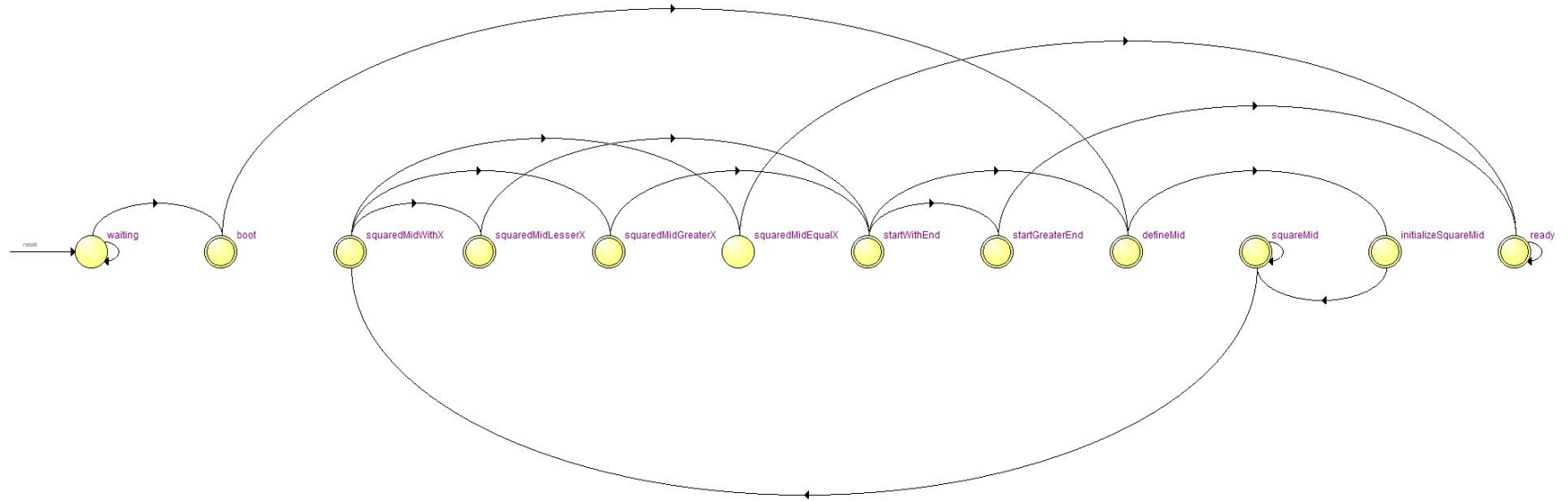

# Resultados de síntese

N = 4

## Slow Model Fmax Summary

	Fmax	Restricted Fmax	Clock Name	Note
1	237.59 MHz	237.59 MHz	clk	

## Flow Summary

Flow Status	Successful - Wed Dec 09 20:04:34 2020
Quartus II 64-Bit Version	13.0.0 Build 156 04/24/2013 SJ Web Edition
Revision Name	sqrt
Top-level Entity Name	sqrt
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	96 / 33,216 ( < 1 % )
Total combinational functions	89 / 33,216 ( < 1 % )
Dedicated logic registers	67 / 33,216 ( < 1 % )
Total registers	67
Total pins	12 / 475 ( 3 % )
Total virtual pins	0
Total memory bits	0 / 483,840 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 70 ( 0 % )
Total PLLs	0 / 4 ( 0 % )

## Analysis & Synthesis Resource Usage Summary

	Resource	Usage
1	Estimated Total logic elements	107
2		
3	Total combinational functions	89
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	19
2	-- 3 input functions	45
3	-- <=2 input functions	25
5		
6	▼ Logic elements by mode	
1	-- normal mode	72
2	-- arithmetic mode	17
7		
8	▼ Total registers	67
1	-- Dedicated logic registers	67
2	-- I/O registers	0
9		
10	I/O pins	12
11	Embedded Multiplier 9-bit elements	0
12	Maximum fan-out node	clk
13	Maximum fan-out	67
14	Total fan-out	465
15	Average fan-out	2.77

# Resultados de síntese

N = 8

Slow Model Fmax Summary				
	Fmax	Restricted Fmax	Clock Name	Note
1	222.27 MHz	222.27 MHz	clk	

Flow Summary	
<b>Flow Status</b>	Successful - Wed Dec 09 19:08:19 2020
Quartus II 64-Bit Version	13.0.0 Build 156 04/24/2013 SJ Web Edition
Revision Name	sqrt
Top-level Entity Name	sqrt
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Final
Total logic elements	151 / 33,216 ( < 1 % )
Total combinational functions	143 / 33,216 ( < 1 % )
Dedicated logic registers	112 / 33,216 ( < 1 % )
Total registers	112
Total pins	20 / 475 ( 4 % )
Total virtual pins	0
Total memory bits	0 / 483,840 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 70 ( 0 % )
Total PLLs	0 / 4 ( 0 % )


Analysis & Synthesis Resource Usage Summary		
	Resource	Usage
1	Estimated Total logic elements	177
2		
3	Total combinational functions	143
4	▼ Logic element usage by number of LUT inputs	
1	-- 4 input functions	33
2	-- 3 input functions	78
3	-- <=2 input functions	32
5		
6	▼ Logic elements by mode	
1	-- normal mode	110
2	-- arithmetic mode	33
7		
8	▼ Total registers	112
1	-- Dedicated logic registers	112
2	-- I/O registers	0
9		
10	I/O pins	20
11	Embedded Multiplier 9-bit elements	0
12	Maximum fan-out node	clk
13	Maximum fan-out	112
14	Total fan-out	776
15	Average fan-out	2.82

# Resultados de síntese


	N = 4	N = 8
Clock	237.59 MHz	222.27 MHz
Logic elements (normal)	72	110
Logic elements (arithmetic)	17	33
Registradores	67	112
Atraso crítico	4.209 ns	4.500 ns
Pior caso em ciclos	83	243



# Resultados de Validação

 

# Resultados de Validação

 

# Análise Crítica